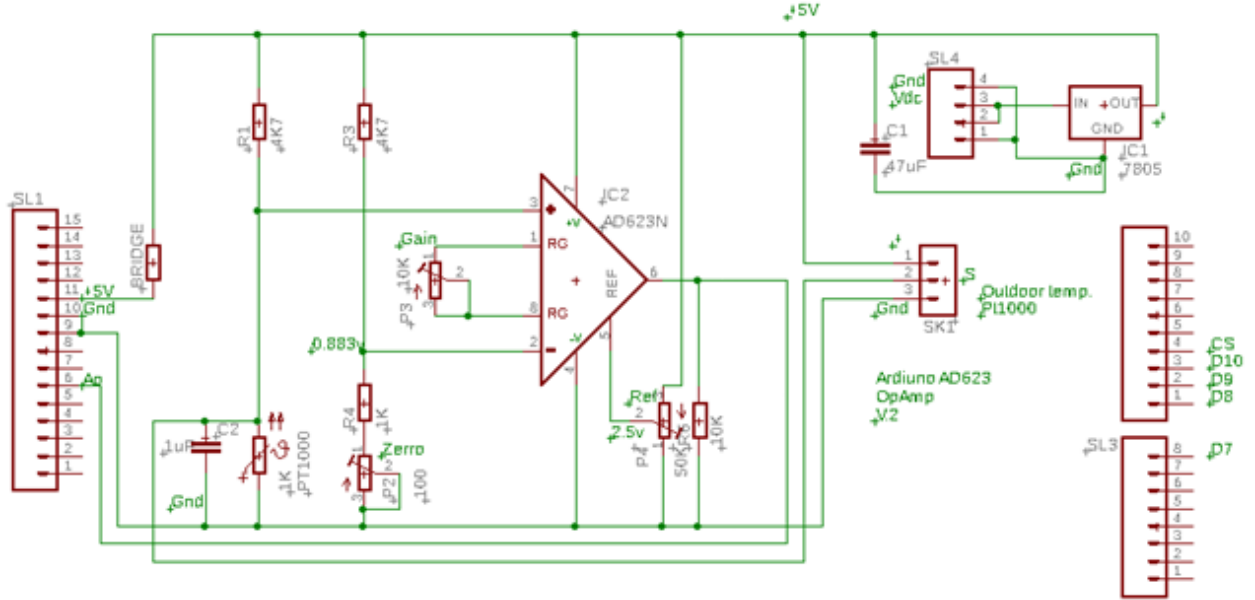


Op-Amp shield

The op-amp shield is to be use for the "Arduino UNO". This project is made to be use with a two wired Pt1000 temperature sensor. Up to five shields can be fit over each other.

The circuit diagram




Component list

Arduino UNO R3




PCB

AD623_OpAmp_V2.brd

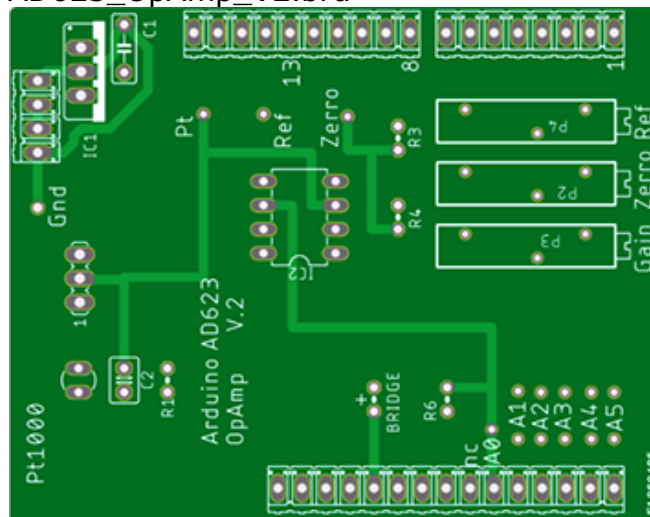


Op-amp
AD623

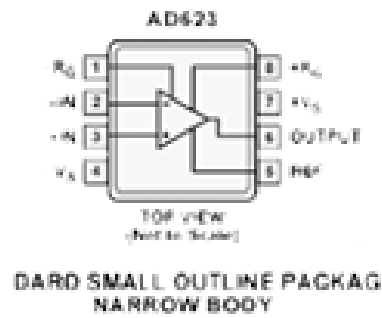

Capacitors
47uF
1uF



Resistors
1kΩ
4.7kΩ
10kΩ

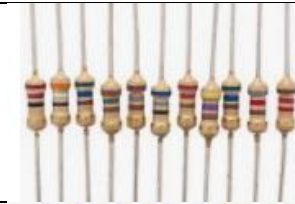

Trim potentiometer
100Ω 1x
10kΩ 1x
50kΩ 1x



ArduinoUNO
connectors




Female precision
header



Female header



PCB layout

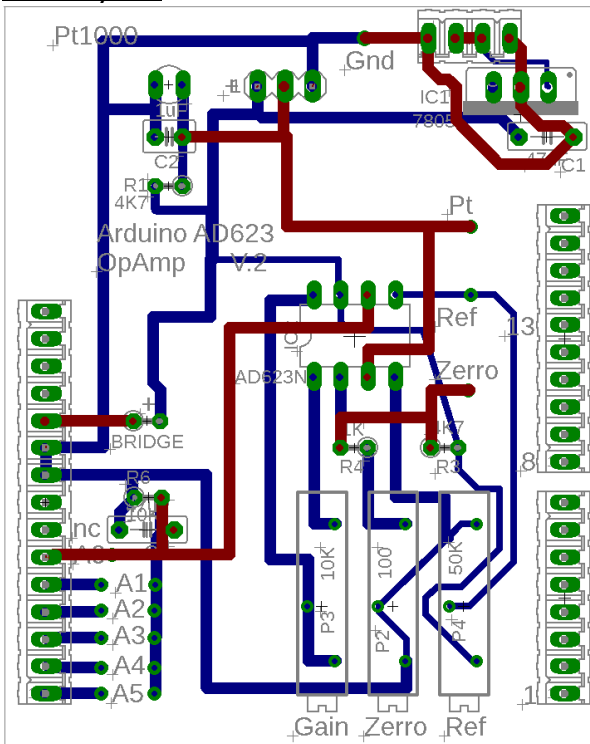

Several Op-Amp shields can be fitted up to 6, the initial shield is connect to "A0". For fitting more boards over each other the hole for "A0" should be drilled out and to solder a wire bridge over "A1" or other.

The "BRIDGE" has to be made if the power comes from the Arduino board.

Test points for adjustments are: Gnd, Pt, Ref and Zerro.

PCB board

Download: [AD623_OpAmp_V2.brd](#)
(Eagle application required)

Sketch

```
// Pt1000 & AD623 TEST
// **** only for one board ****;
float Vout0; //analoge input A0
float Volt0; //analoge voltage input A0
float Temp; // decimaal berekende temperatuur

void setup() {
  Serial.begin(9600); // baud rate serial port (USB)
}

void loop() {
  Vout0 = analogRead(A0);
  Volt0 = ((Vout0*50/1024)-25)*2.68;
  Temp = Volt0;
  Serial.print ("Vout-0 = ");
  Serial.print (Vout0);
  Serial.print (" Volt-0 = ");
  Serial.print (Volt0);
  Serial.print (" Temp =");
  Serial.print (Temp);
  Serial.println();

  delay (1000);
}
```